

## Homework 4: Synthesis

### (A) sel\_sense

You can use the behavioral code that you wrote for sel\_sense in Homework Assignment #3 for the questions that follow, or you can use the behavioral code in /cad\_area/vlsi/design/selsense/sel\_sense.v.

#### Submissions:

- (i) Synthesize sel\_sense with the SkyWater HS and MS libraries. Submit the resulting netlists.
- (ii) Put a “don’t use” on all XOR and XNOR gates, resynthesize, and submit the resulting netlists.
- (iii) For the HS and MS netlists with no “don’t use” directives, plot A->B delay as a function of load capacitance at B. Let the capacitance vary from 0.005 to 0.1 pF. Create plots for S = 0 and for S = 1. Let transition time at A be 0.04 ns. Note that for timing to be reported from A to B, you will need to specify a max delay constraint for that path.

### (B) mux\_comparator

#### Submissions:

- (i) Write behavioral Verilog code for a combinational logic function called “mux\_comparator” that compares two three-bit numbers x and y, and outputs whichever one of the two numbers is numerically less. Output should be called z.
- (ii) Synthesize this function with the libraries Cadence RAK, NangateOpenCellLibrary and Nangate\_15nm\_OCL (see Homework #1 for paths). Submit the three netlists that result.
- (iii) In each case, identify the critical path from input to output, listing the max\_delay from input to output. List the number of standard cells in the critical path.
- (iv) In each case, identify the min\_delay path and tabulate the min delay. List the number of standard cells in the min\_delay path.
- (v) Change the three-bit numbers x and y to eight-bit numbers. Resynthesize, and report the number of standard cells in the critical (max\_delay) path.