

**Name – Manjunath Veeraiah Kalmath**

**USN - 01FE17BEC240**

**Roll No – 175**

**School of ECE**


Q1. Write a simple behavioral Verilog code for sel\_sense

\*\*\*\*\*Verilog Code\*\*\*\*\*

```
Module sel_sense(A,S,B);  
Input A,S;  
Output B;  
always@(*)  
begin  
    if(S==0)  
        B=A;  
    else  
        B=!A;  
end  
endmodule
```

\*\*\*\*\*

 Q2. Draw a schematic of a circuit that implements sel\_sense. Your schematic must involve gates like NAND2, NOR2, MUX, INVERTER, XOR, NAND, etc. Choose whichever gates you like to implement the logic. Do not make a truth-table; draw a schematic based only on your understanding of the logic. Use standard symbols for the gates in your schematic.



Q3. Now write a truth table for the circuit. Based on your truth-table, if you would like to make an alternative schematic for the circuit, please do so, and you can submit that schematic as well.

→ Truth Table:

I/p		O/p
A	S	B
0	0	0
0	1	1
1	0	1
1	1	0

From Truth Table

$$B = A \oplus S.$$

⇒ Use of "XOR Gate"

→ Schematic After writing Truth Table:

